

Lab Assignment #6

Copyright©2006 by Steven P. Levitan

**University of Pittsburgh, Department of Electrical and Computer Engineering
(Friday, Week 6)**

Assignment (due Friday, October 15, 2008)

Add more cells to your standard cell library:

1. Schematic design a Flip-Flop as shown in Figure 7.19(b) in the 3rd edition of the book, which is figure 10.19(b) in the fourth edition.

Notes:


- A. The pass gates do not have any connections to power or ground, none the less they must have well/substrate contacts in the well.
- B. Carefully observe and label the two clock phases necessary
- C. Add two inverters to the FF cell one to buffer clock and one to create phi_bar ($\sim\phi$)

2. Schematic design a Flip-Flop as shown in Figure 7.21 (or 10.21) in the book.

Notes:

- A. Carefully observe and label the four (4) clock phases necessary
- B. Add four inverters to the FF cell to buffer the clock and create phi1_bar ($\sim\phi_1$), phi1_bar2 ($\sim\phi_2$)

 3. Schematic design a Flip-Flop as shown below from four And-Or-Invert gates and 3 inverters:



- 4.

- A. For Flip-flop 1 and 3 measure the setup time for both rising and falling inputs and include the T_{CQ} vs. T_{DC} plots to show the clock to output delay as a function of the clock setup time.
- B. For Flip-flop 1 and 3, measure the hold time for both rising and falling inputs and include the T_{CQ} vs. T_{DC} plots to show the clock to output delay as a function of the clock hold time.
HINT: you need another edge on D after the clock rising edge, which restores D to its starting value. T_{DC} here should be the delay from clock rising edge to this second edge of D. Make a large enough setup-time to not affect your hold time measurement!
- C. For FF 1 and 3, plot T_{DQ} vs. T_{DC} for both rising and falling inputs to show the input to output delay. Find the optimum setup time with minimum D to Q delay.

- D. For each of FF 1 and 3, if their hold times are negative (a changing D can still pass through the FF, it does not hold its value after clock rising edge) explain why.
 - E. For FF 2, find out how much overlap between Phi1 and Ph2 makes it fail.
 - F. For FF 1, you may find that its performance is worse (larger setup and hold time) for a falling input. Describe how you can skew the 4 inverters along the main path to balance the performance for rising and falling inputs.
5. Pick either FF 1 or FF 3 and lay it out as a standard cell. Explain the reasons for your choice, including, but not limited to, the setup and hold times.